

END TERM EXAMINATION

THIRD SEMESTER [B.TECH.]– DECEMBER 2008

Paper Code: ETEE203

Paper ID: 29203

Time : 3 Hours

Subject: Analog Electronics-I

(Batch: 2004-2007)


Maximum Marks : 75

Note: Attempt five questions in all including Q.1 which is compulsory.

- Q.1 Answer the following: - (2.5x10=25)
- Discuss the effect of temperature on the V-I characteristics of a pn-junction diode.
 - Explain the difference in metals, semiconductors and insulators with the help of energy band diagram.
 - Define α , β and I_{CBO} and I_{CEO} .
 - Explain how cut-off condition is achieved in a transistor.
 - An emitter follower is used as a buffer. Explain.
 - Explain why voltage gain is stabilized in a CE amplifier if a resistance R_E is placed in the emitter branch.
 - Explain 'Base Width Modulation'.
 - Discuss the advantages of negative feedback in amplifiers.
 - Show that the gain falls-off at the rate of 6dB/octave, in an RC-coupled amplifier.
 - Give the advantages of FET over BJT.


UNIT-I

 - Q.2 (a) Explain the storage time effects in a pn-jn diode if the voltage applied to a diode is changed from $+V_F$ to $-V_R$. (6)
- (b) In the circuit shown in Fig.1, the silicon diode has $V_T = 0.6V$, $R_F = 10\Omega$, determine (i) the total voltage across R_L , (ii) the total current, i_D . (6.5)




OR

- Q.3 (a) For a step graded pn junction, prove that the transition capacitance, C_T is given by
- $$C_T = A \left[\frac{q\epsilon N_A}{2 V_T} \right]^{1/2}; \text{ for } N_A \gg N_D \quad (6)$$
- (b) A 9V zener is used in the circuit shown in Fig.2. The load current is to vary from 12 to 100 mA. Find the value of the series resistor R and $I_{Z,max}$. The input voltage is constant at 20V and $I_{Z,min} = 10mA$. (6.5)

 **UNIT-II**

 - Q.4 (a) Show the various regions of operation on the output characteristics of a transistor in CE configuration. Explain the shape of the curves quantitatively. (6)
- (b) Analyse the circuit shown in Fig.3 to find the region of operation. Assume $\beta_F = 100$, $V_{BE,active} = 0.7V$, $V_{BE,sat} = 0.8V$, $V_{CE,sat} = 0.2V$. (6.5)




P.T.O.

[-2-]


OR

 - Q.5 (a) Prove that a self-bias circuit is better than a fixed bias circuit. (6)
 (b) For the circuit shown in Fig.4, a silicon transistor with $\beta = 50$ at 25°C is used. It is desired that $V_{CE} = 5\text{V}$. Determine (i) R_B , (ii) the stability factor $S(I_{CO})$ (iii) the value of I_C at 100°C , if $\Delta I_{CO} = 19.9\text{mA}$. (6.5)




UNIT-III

 - Q.6 (a) Prove that : $h_{ic} = h_{ie}$; $h_{rc} = 1$
 $h_{ic} = -(1+h_{ie})$; $h_{oc} = h_{oe}$ (6)
 (b) The transistor in the amplifier shown in Fig.5 has the following parameters: $h_{ie} = 2\text{k}\Omega$; $h_{ie} = 50$; $h_{re} = 2 \times 10^{-4}$; $h_{oe} = 20 \times 10^{-6}\text{A/V}$. Determine: A_v , A_{vs} , R_i and R_o . Given $\beta = 200$. (6.5)



OR

 - Q.7 (a) Explain the various components in a Hybrid- π model of a transistor at high frequencies. Define f_β & f_T and find the relation in these parameters. (6)
 (b) A two stage amplifier is shown in Fig.6. Both the transistors are identical and have the parameters: $h_{ie} = 100$ and $h_{ie} = 1\text{k}\Omega$, $h_{oe} = 0$, $h_{re} = 0$. Determine the overall voltage gain. (6.5)



UNIT-IV

- Q.8 (a) Explain the effect of negative feedback on the input and output impedances of an amplifier using voltage series feedback. Derive the generalized expression. (6)
 (b) Explain the construction, drain and transfer characteristic of n-channel enhancement and depletion-type of MOSFETs. (6.5)
 OR
 Q.9 (a) Discuss the various advantages of negative feedback in amplifiers. Draw a circuit that uses (i) voltage shunt feedback (ii) current series feedback. (6.5)
 (b) Explain (i) fixed-bias (ii) self-bias arrangement for biasing a JFET. (6)
