


**FIRST TERM EXAMINATION**

III<sup>rd</sup> Semester [B. Tech.]  
 Paper Code: ETEC-207  
 Time: 1½ Hrs.

September 2008  
 Sub: Analog Electronics- I  
 Max. Marks: 30

Note: Attempt Q. No. 1 and any two more questions.

 - Q. 1 (a) Prove that the depletion width  $W$  is proportional to the square root of total junction voltage in a reverse biased junction diode. (3)
- (b) Draw the Ebers Moll model of a PNP transistor. Obtain equations for  $I_C$  &  $I_E$  (3)
- (c) Explain the Early effect in transistors. (2)
- (d) Explain the temperature dependence of  $V/I$  characteristics of a diode. (2)
- Q. 2 (a) Explain the switching behavior of a P-N junction diode when the input voltage changes from  $+V_F$  to  $-V_R$ . Discuss how storage time can be reduced. (5)
- (b) Design a zener voltage regulator that will maintain an output voltage of 20 V across 1 k $\Omega$  load, when the input voltage range in 30-50 V. Determine  $R_S$  & maximum zener voltage. (5)
- Q. 3 (a) A half wave rectifier, having a load of 1 K $\Omega$ , rectifies an alternating voltage of 325 V peak value & the diode has a forward resistance of 100  $\Omega$ . Calculate (a) Average value of current. (b) D. C. power output, (c) Efficiency of the rectifier. (3)
- (b) Write a short note on LED. (2)
- (c) Determine the region of operation for the circuit shown. Assume typical values (5)



- Q. 4 (a) Explain the saturation and cut off condition in a CE connected transistor. (5)
- (b) The voltage at emitter,  $V_E = -5$  V,  $V_{BE} = 0.7$  V, find  $V_B$ ,  $V_C$ ,  $\alpha$ ,  $\beta$  for the circuit shown. (5)

