
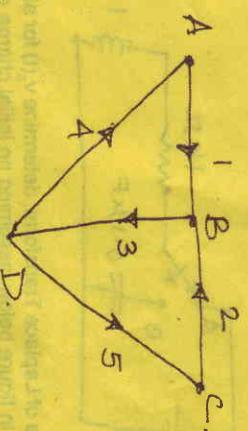


**Question 4** A node is a point from which at least one branch originates. A junction is a point where two or more branches meet. Mesh is a closed loop formed by the sides of a polygonal region. Loop is a closed path formed by the sides of a polygonal region. Tree is a connected graph with no cycles. Co-tree is a set of edges which, when added to the tree, will form a spanning tree.

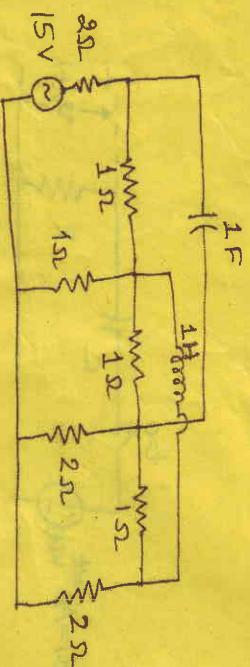
- (a) Differentiate between: node & junction, mesh & loop, tree & co-tree, with the help of examples. For the graph shown in the figure below, draw an arbitrary circuit, given that A, B, C & D are nodes and 1 to 5 are branches. (3)




- (b) For the given bridged - ladder circuit, draw the graph and selecting the branches having  $1\ \Omega$  resistances as the twigs, write down the cut-set and tie-set matrices. (3)



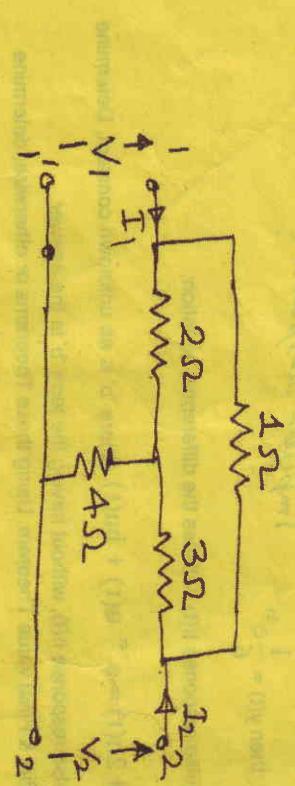- (c) Find the short-circuit admittance parameters for the given bridged - T network: (4)



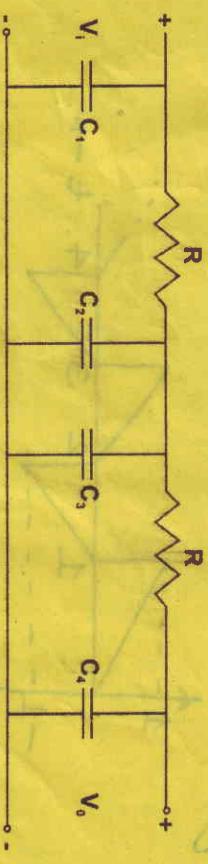- (g) For the circuit shown in the figure, the order of the differential equation relating  $v_o$  &  $v_i$  is to be found. Without writing down the equations, find out the order and give reason for your answer.



[4]

(Please write your Roll No. immediately)

Exam Roll No.: ..... 031.....

## FIRST – TERM EXAMINATION

Third Semester (B.Tech.) – September 2007

Time : 1 Hr. 30 Min.


Paper Code : ETEC205

Subject : Circuits & Systems  
Maximum Marks : 30

Note: Question No. 1 is compulsory. Attempts two more questions.

Question 1 (Compulsory)

(1x10)

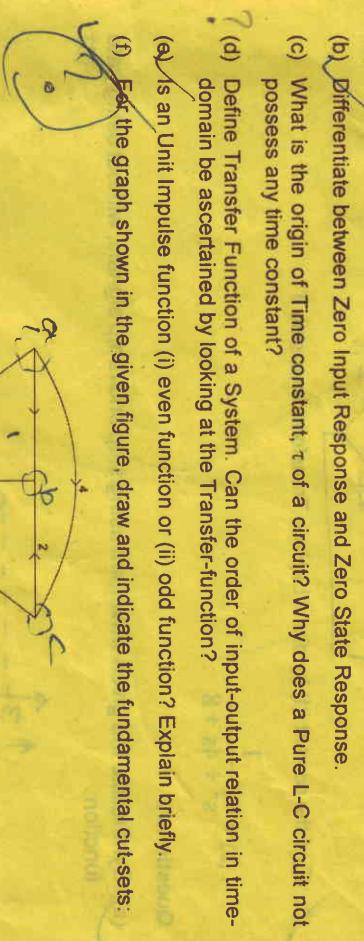

- (a) What are active sources and passive elements?  
(b) Differentiate between Zero Input Response and Zero State Response.  
(c) What is the origin of Time constant,  $\tau$  of a circuit? Why does a Pure L-C circuit not possess any time constant?

- (d) Define Transfer Function of a System. Can the order of input-output relation in time-domain be ascertained by looking at the Transfer-function?


- (e) Is an Unit Impulse function (i) even function or (ii) odd function? Explain briefly.

- (f) For the graph shown in the given figure, draw and indicate the fundamental cut-sets:

[1]



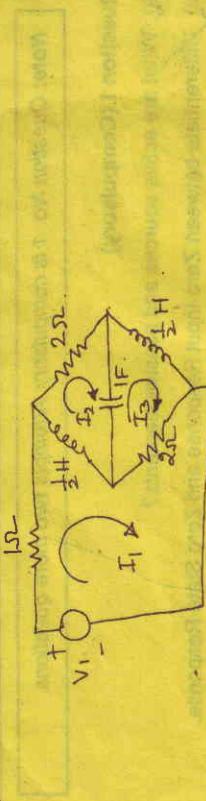(i) For the network shown in the figure, write down the loop-basis transform equations that describe the system when all initial conditions are zero.




(ii) Find the current  $i(t)$  by direct Laplace Transform Inversion if

$$I(s) = \frac{1}{s^2 + 4s + 8}$$

Questions 2 (a) Synthesize the given waveform using step and ramp signals, without using gate function:



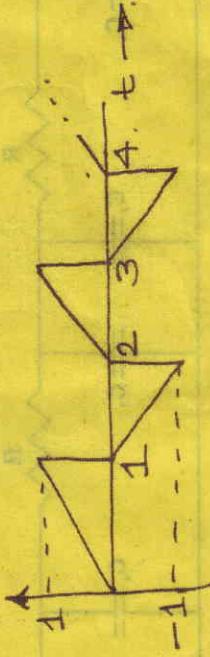
(b) Find the Laplace Transform of the periodic Waveform shown in the figure below:



(c) In the given circuit shown below, switch S is changed from position A to B at  $t = 0$ .

Determine the values of  $i$ ,  $\frac{di}{dt}$  &  $\frac{d^2i}{dt^2}$  at  $t = 0$  using classical method of transient analysis.

(4)

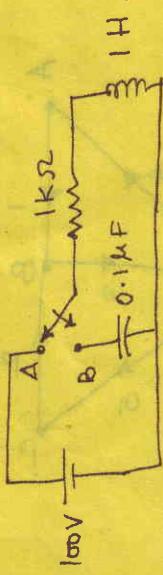


Question 3

(a) Using the technique of Laplace Transform, determine  $v_o(t)$  for all  $t \geq 0$  after switching ON of the circuit given in figure below, assuming no initial charge on the capacitor, for the conditions

$$(i) \alpha \neq \frac{1}{RC}$$

$$(ii) \alpha = \frac{1}{RC}$$

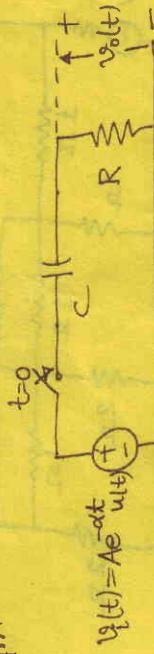

(b) A causal LTI system with impulse response  $h(t)$  has the following properties;

(i) When the input to the system is  $x(t) = e^{2t}$ , then  $y(t) = \frac{1}{6}e^{2t}$ . Impulse response?

(ii) The impulse response  $h(t)$  satisfies the differential equation:

$$\frac{dh(t)}{dt} + 2h(t) = e^{-4t} u(t) + bu(t) \text{ where } 'b' \text{ is an unknown constant. Determine the impulse response } h(t), \text{ without having the term } 'b' \text{ in the answer.}$$

(c) State Initial & Final value Theorem. Using these Theorems or otherwise, determine the initial and final values of current  $i(t)$ , given that  $I(s) = \frac{5(s^2 + 2s + 1)}{s(s^2 + 7s + 6)}$

$$(2)$$

[2]

[3]

Q.4.

(Please write your Roll No. immediately) Exam Roll No.: 031**SECOND – TERM EXAMINATION**

Third Semester (B. Tech.) – November 2007

Time: 1 Hr. 30 Min.

Maximum Marks: 30

- Q.4.** (i) State whether the given polynomial is Hurwitz or not? [2x2.5]

(a)  $p(s) = s^5 + s^4 + 2s^3 + 2s^2 + s + 1$

- (ii) Determine whether the function

$F(s)$  is a p.r.f. or not?

$$F(s) = \frac{s^3 + s^2 + 2s + 1}{s^4 + s^3 + 3s^2 + s + 1}$$

- (b) Write short notes on any **Two** of the following:

- (i) Tellegen's Theorem.
- (ii) Permissibility of Interconnection for two 2 port networks
- (iii) Network functions.

\*\*\*

- Q.No.1** (a) State the conditions for (i) Symmetrical (ii) Reciprocal two-port networks in terms of ABCD parameters and hybrid parameters.

(b) Show that  $[Y]_{2 \times 2}^{-1} = [Z]_{2 \times 2}^{-1}$  for a two port network.

- (c) State Millman's Theorem as applied to A.C. networks for both voltage & current sources.


- (d) Write down the limitations of Thevenin's Theorem with brief explanation.

- (e) List the necessary & sufficient conditions for a function to be a positive real function.

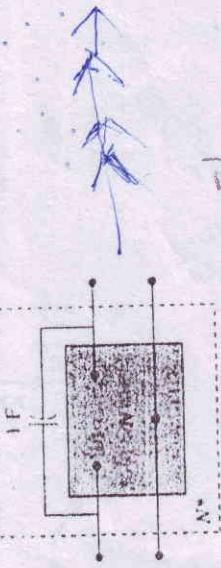- (f) For the two port Network, N shown in figure below, the open circuit impedance parameters are

$$Z_{11} = 7\Omega, Z_{12} = 2\Omega, Z_{21} = 10\Omega \text{ & } Z_{22} = 3\Omega$$

Find the short circuit admittance parameters of the new two-port network N represented by dotted box, represented by  $N^*$



$$Y_A = \begin{bmatrix} 5 & -5 \\ -5 & 5 \end{bmatrix}$$


$$Y_B = \begin{bmatrix} 7 & 2 \\ 10 & 3 \end{bmatrix}$$

$$= \frac{1}{11} \begin{bmatrix} 7 & 2 \\ 10 & 3 \end{bmatrix} - \frac{1}{2} \begin{bmatrix} 5 & -5 \\ -5 & 5 \end{bmatrix}$$


$$= \begin{bmatrix} 5 & 2 \\ 10 & 3 \end{bmatrix}$$

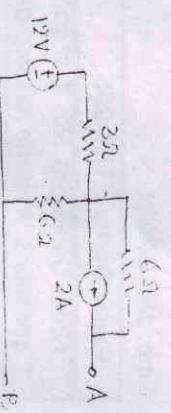- (g) For question 1(f) convert the final admittance parameters to an equivalent circuit representing hybrid parameters.

Short circuit  
to  
hybrid  
parameters  
conversion)



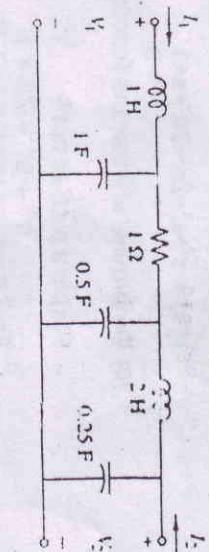- (b) Find the inverse Transmission parameters of the circuit of the given two port network, using properties of interconnection. [5]




Q.3.

- (a) For the given A.C. circuit, find the currents following through the impedances  $\bar{Z}_1, \bar{Z}_2$  and  $\bar{Z}_3$  using Superposition Theorem given that  $\bar{Z}_1 = (3 + j4)\Omega$ ,  $\bar{Z}_2 = (5 - j12)\Omega$  and

$$\bar{Z}_3 = (6 + j14.4)\Omega.$$

- Q.2. (i) Is the polynomial  $s^5 + s^3 + s$  a Hurwitz polynomial? [5]

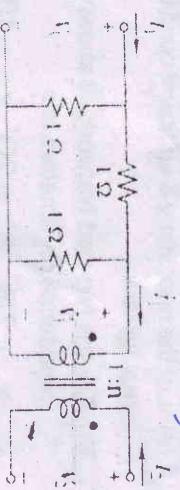
- (a) Show that for the given two-port network:



The Y parameters matrix is given by

$$[Y] = \begin{bmatrix} 2 & -\frac{1}{n} \\ -\frac{1}{n} & \frac{2}{n^2} \end{bmatrix}$$

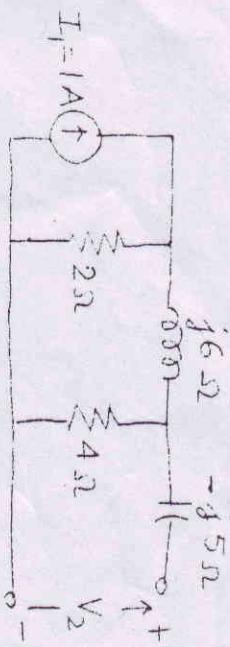- (c) Verify Reciprocity Theorem in the network given below:



- (b) State Maximum Power Transfer Theorem. Derive the relation between maximum power delivered to the impedance,  $Z_L = R_L + jX_L$ .

# END-TERM EXAMINATION

THIRD SEMESTER [B.TECH.] - DECEMBER-2007

Paper Code: ETEC-205(Batch-2004-2006)

Subject: Circuits and Systems

Paper Code: 28205

Time : 3 Hours

Maximum Marks : 75

Note: Attempt any five questions including Q.No.1 which is compulsory. Symbols have their usual meanings.

Q.1 Choose the best or correct alternative in the following: -

- (a) The sinusoidal signal  $x[n]$  has fundamental period  $N = 5$  samples. The smallest angular frequency for which  $x[n]$  is periodic, given by: - (2)

- (i)  $\frac{\pi}{5}$  rad/cycle      (ii)  $\frac{3\pi}{5}$  rad/cycle  
 (iii)  $\frac{2\pi}{5}$  rad/cycle      (iv)  $\frac{\pi}{6}$  rad/cycle

- (b) For the current and voltage variables that are defined in Fig.1, state which of the circuits shown are characterized by the equation  $v(t) = -R i(t)$ . (2)

- (i) circuit 1    (ii) circuit 2    (iii) circuit 3    (iv) some other answer

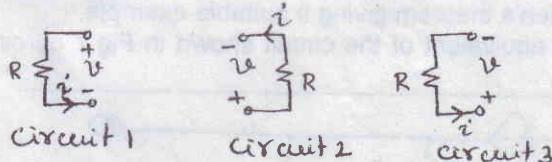


Fig - 1

- If a charged, linear, time-invariant capacitor is connected in parallel with an uncharged one, what is the waveform of the charging current: - (2)

- (i) a step    (ii) a ramp    (iii) an impulse    (iv) an exponential

The Thevenin's voltage  $v_{th}$  in the circuit of Fig.2 is: - (2)

- (i) 4V    (ii) 2V    (iii) 2.5V    (iv) 0.1V

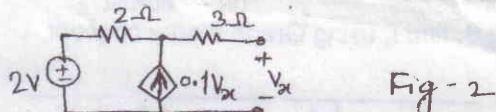


Fig - 2

- (e) In order that  $f(t)$  be Laplace transferable, it is sufficient that: - (2)

(i)  $\int_0^\infty |f(t)| \cdot e^{-\sigma t} dt > \infty$       (ii)  $\int_0^\infty |f(t)| e^{\sigma t} dt < \infty$

(iii)  $\int_0^\infty |f(t)| e^{\sigma t} dt < \infty$       (iv)  $\int_0^\infty |f(t)| e^{\sigma t} dt > \infty$

- (f) For the circuit shown in Fig.3. (3)

- (i) transmission parameters do not exist  
 (ii) h-parameters do not exist  
 (iii) z-parameters do not exist  
 (iv) none of the above

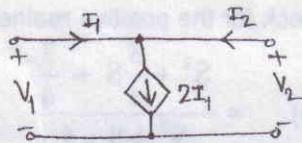


Fig - 3

- (g) The input admittance of an LC network must have: - (2)

- (i) a zero at infinity  
 (ii) a pole at infinity  
 (iii) neither a pole nor a zero at infinity  
 (iv) either a pole or a zero at infinity

- Q.2 (a) Show that any arbitrary sequence can be represented as a linear combination of shifted unit impulses. (7)

- (b) For the circuit shown in Fig.4, the switch 'SW' is opened at  $t = 0$ , find  $v_c(t)$  for  $t \geq 0$ . (8)

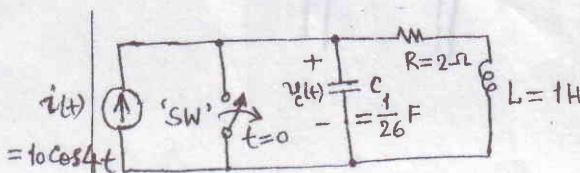


Fig - 4

[-2-]

Q.3 (a)

Write the equation of the waveform shown in Fig.5, in terms of steps, ramp and other related functions. (7)

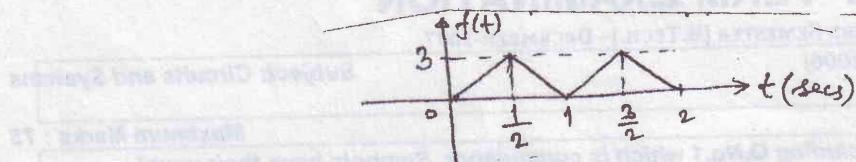


Fig - 5

(b)

Show that for the circuit of Fig.6 (for  $\beta = 1$ ). (8)

$$h_{21} = \frac{R_A}{R_B}$$

$$h_{22} = 0$$

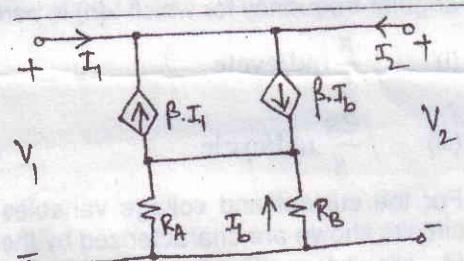


Fig - 6

Q.4

(a)

State and explain Tellegen's theorem giving a suitable example. (7)

(b)

Determine the Norton's equivalent of the circuit shown in Fig.7 across the terminals (a) – (b). (8)

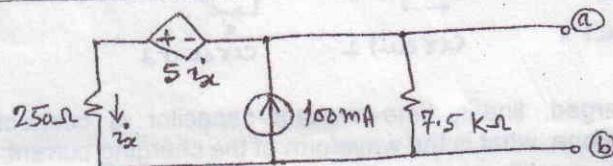


Fig - 7

Q.5

(a)

Explain the following: - (3+2+2)

(b)

(i) Isomorphic graphs (ii) cutest

In the circuit of Fig.8, find  $i_x$  using Graph theory concept. (8)

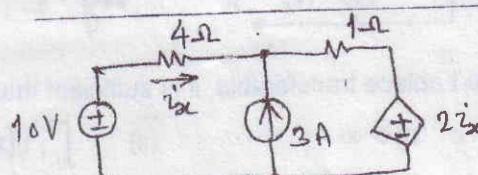


Fig - 8

Q.6

(a)

Check for the positive realness of the following function: - (7)

$$F(s) = \frac{s^2 + \frac{3}{4}s + \frac{3}{4}}{s^2 + s + 4}$$

(b)

The impedance of an RC network is sketched for real values of S as shown in fig.9. What is  $Z_{RC}(S)$ ? Synthesize  $Z_{RC}(s)$  in Foster's second form. (8)

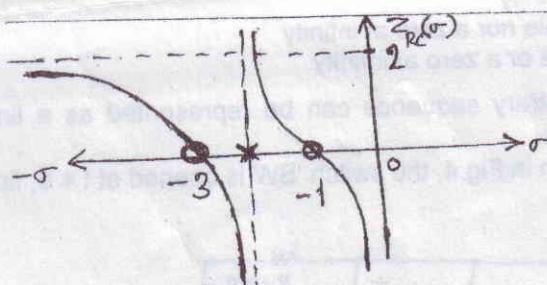


Fig - 9